




Sheet 1


1. Please draw the minimum CMOS transistor network that implements the functionality of Boolean equation $F = ((A+B) C + D)'$. You can assume both the original and complemented versions of each literal are available as gate inputs.

2. Please draw the minimum CMOS transistor network that implements the functionality of Boolean equation $F = (A (B C + D))'$. You can assume both the original and complemented versions of each literal are available as gate inputs.

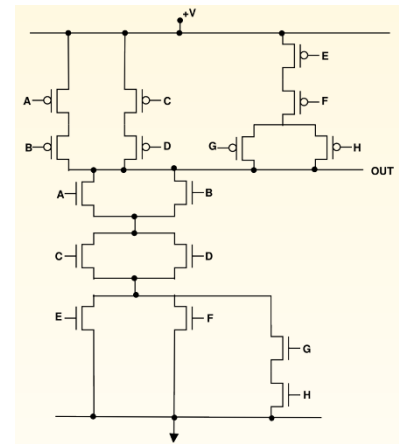
3. find output expression for the following CMOS transistor network?



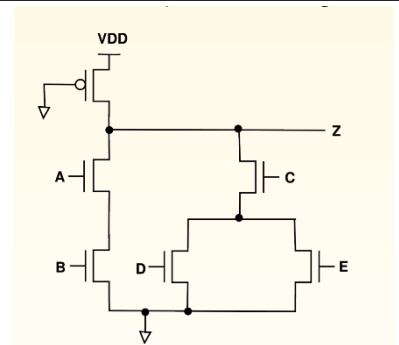4. Find output expression for the following CMOS transistor network?




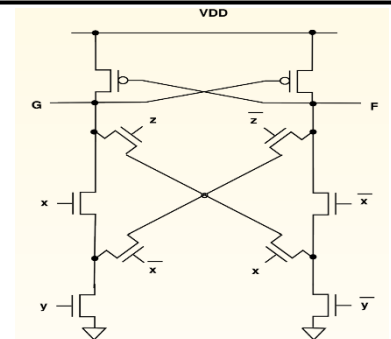5- Find output expression for the following CMOS transistor network?





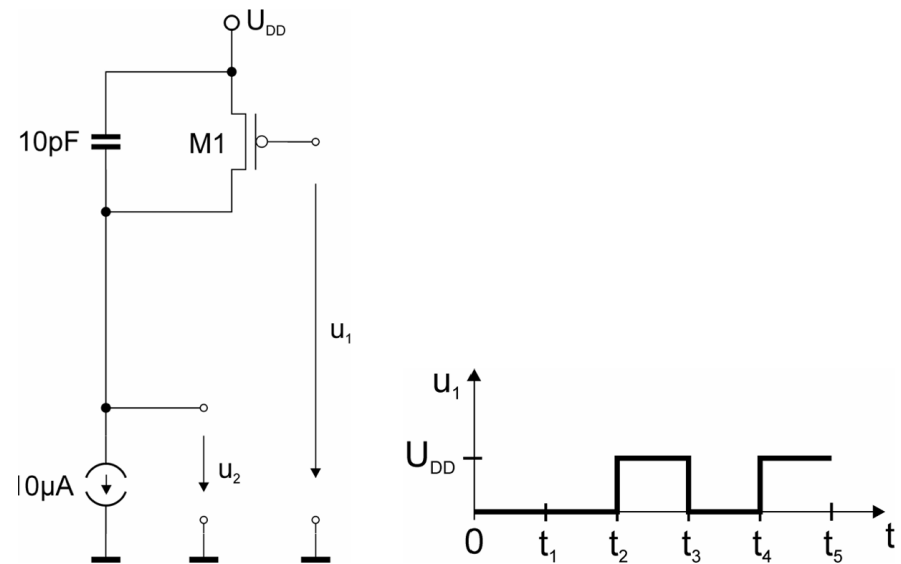6- The circuit in Figure with $U_{DD}=5\text{ V}$ and the time course $u_1(t)$ in Figure 4.2 with $t_1=2\mu\text{s}$ are given. Draw the time course $u_2(t)$ in the area $t_1>t>t_5$! Note: The resistance of a conducting transistor is negligible



7- For the following circuit, Sketch the output waveform as function of input waveform.

